

**Scottish Church College**  
**Internal Assessment Examination, 2021**  
**Basic Electronic Devices and Circuits**  
**Semester II (Hons.)**  
**CMSA**  
**Paper: CC-4**

**Time: 1 Hour**

**Full Marks: 30**


**Answer Question 1 and any four (4) from the rest.**

- 1. Answer any four questions (1.5 x 4)**
  - i. List out the ideal characteristics of OPAMP.
  - ii. List the basic blocks of IC 555 timers.
  - iii. Why must the base be narrow for the transistor (BJT) action?
  - iv. What is multiplying DAC?
  - v. List the PN diode parameters.
  - vi. State the maximum power transfer theorem.
  - vii. What is the superposition theorem?
  
- 2.**
  - i. What do you understand about transistor self biasing?
  - ii. What are the factors that affect the bias of a transistor? **[3 + 3]**
  
- 3.**
  - i. Define diffusion capacitance of a diode
  - ii. In your own words, define an intrinsic material, a negative temperature coefficient, and covalent bonding. **[3 + 3]**

4. Define  $\alpha$  and  $\beta$  for a transistor. Derive relation between them. In a CE transistor circuit if  $\beta=100$  and  $I_B=50\mu A$ . Compute the values of  $\alpha$ ,  $I_E$  and  $I_C$ .

[6]

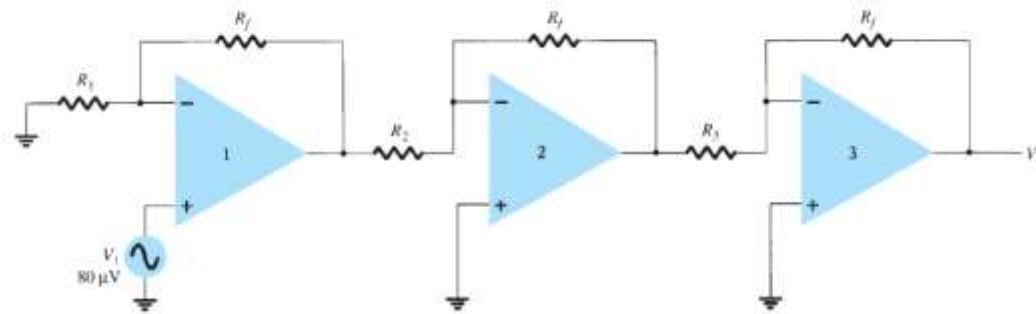5. Calculate the output voltage using the circuit of the figure below for resistor components of value  $R_f = 470\text{ k}$ ,  $R_1 = 4.3\text{ k}$ ,  $R_2 = 33\text{ k}$ , and  $R_3 = 33\text{ k}$  for an input of  $80\text{ mV}$ .




[6]

6. i. Define CMRR of an op-amp.  
 ii. What do you mean by monostable multivibrator?  
 iii. What is multiplying DAC?


[2 + 2 + 2]

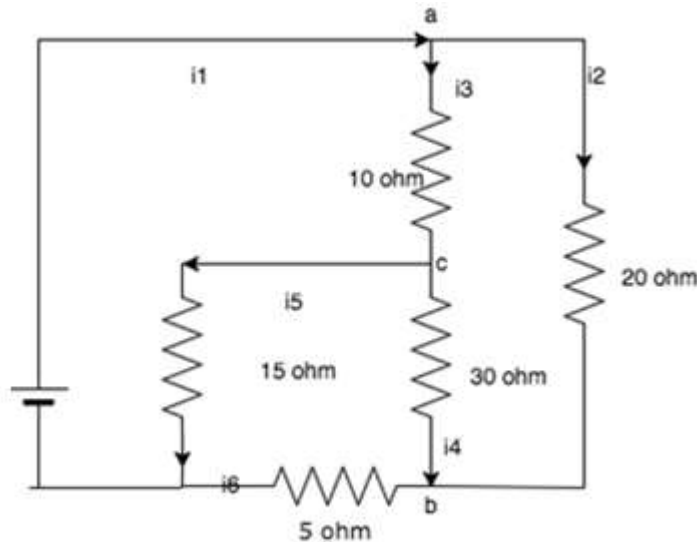7. i. What is KCL?  
 ii. Find the value of  $i_2$ ,  $i_4$  and  $i_5$  given that  $i_1=3\text{ A}$ ,  $i_3=1\text{ A}$  and  $i_6=1\text{ A}$ .




[4 + 2]

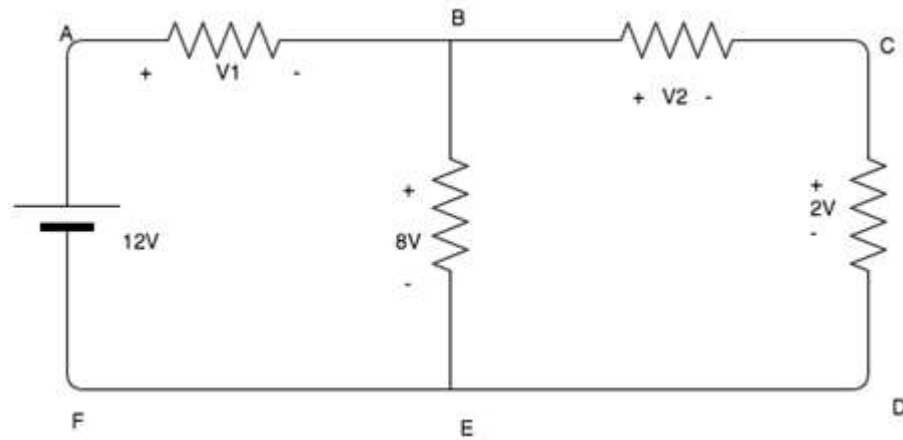8. i. State Kirchhoff's Voltage Law. What physical quantity is conserved by this law?
- ii. Calculate the value of  $V_1$  and  $V_2$ .



[3 + 3]

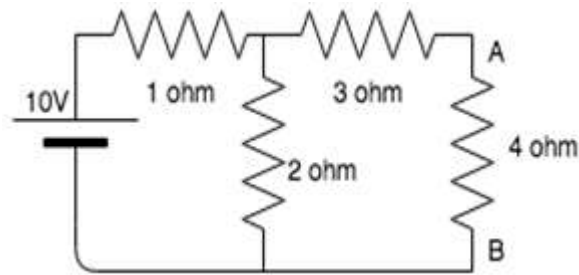9. i. Give Norton's theorem.
- ii. Calculate the Thevenin resistance across the terminal AB for the following circuit:



[2 + 4]